

12. Worksheet: Batteries in series and parallel

It is possible to vary total voltage and current from a number of batteries by connecting them in different ways in the circuit.

In this activity you will investigate the behaviour of batteries connected in series and parallel in dc circuit. Find out what is the purpose of these connections. Plan your own investigation and draw conclusions.

